

High Level Verification using UVM


LAB-1: Setting up simple testbench in verilog for a nibble CPU DUT

Objective:

- To understand DUT specification, design and RTL
- To develop a simple testbench to verify basic operations for nibble CPU DUT
- To understand how to instantiate DUT in testbench
- To generate stimulus to DUT to perform add and multiplication operation

Tasks:

- Understanding the DUT

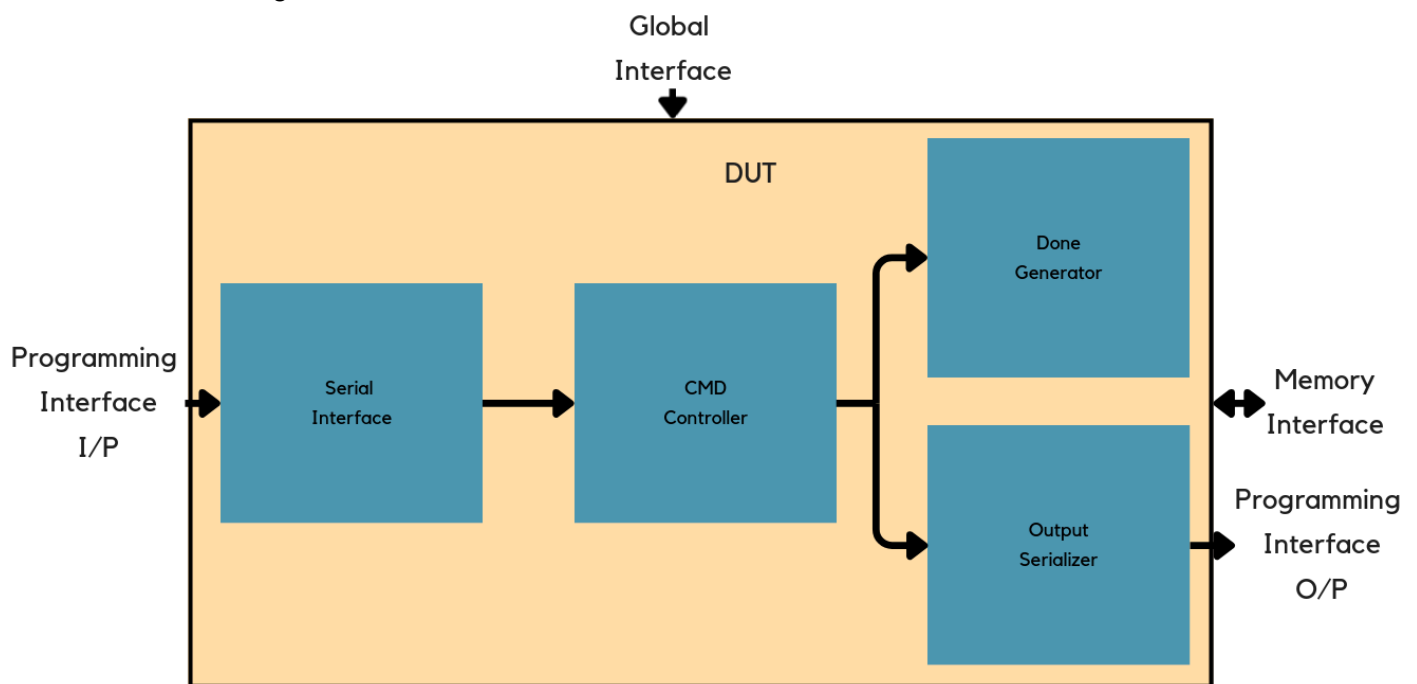

DUT - Nibble CPU System

- **Purpose**
 - Execute memory-mapped instructions.
 - Support 32-bit ADD and MUL.
 - Serialize results as 4-bit nibbles.
- **Top Module - `cpu_top`**

`cpu_top.sv` Interfaces

- **Global Interface:** `clk`, `rst_n`
- **Programming Interface:**

- [3:0] prog_nibble_in
- prog_nibble_in_valid
- [3:0] prog_nibble_out
- prog_out_valid
- prog_done
- **Memory Interface:**
 - [11:0] mem_addr
 - [31:0] mem_wdata
 - [31:0] mem_rdata
 - mem_wen
 - mem_cen

Internal Modules and Their Roles

serial_interface.sv

- **Function:** Input deserialization
- **Operation:**
 - Collects 4-bit nibbles.
 - Assembles 52-bit instruction.
- **Output:**
 - [11:0] frame_addr - Address to be modified or read
 - [7:0] frame_cmd - Command for CPU
 - [31:0] frame_wdata - Data to be written
 - frame_valid

cmd_controller.sv

- **Function:**
 - Central control FSM.
 - Decodes commands.
 - Sequences memory accesses.
 - Performs arithmetic/logical operations.
 - Manages result, errors, and serializer handshaking.
- **Input:**
 - frame_valid - Command available
 - frame_addr[11:0] - Base memory address
 - frame_cmd[7:0] - Opcode
 - frame_wdata[31:0] - Write data
 - frame_ready - Controller idle / ready
- **Result / Status Interface**
 - cmd_start - Command accepted
 - cmd_busy - Controller active
 - cmd_result[31:0] - Operation result
 - cmd_result_valid - Result valid
 - cmd_error - Error occurred
 - cmd_error_type[1:0] - Error classification
 - serializer_busy - Downstream back-pressure
- **Memory Interface**

- `mem_addr[11:0]` - Memory address
- `mem_wdata[31:0]` - Memory write data
- `mem_rdata[31:0]` - Memory read data
- `mem_wen` - Write enable
- `mem_cen` - Chip enable

`output_serializer.sv`

- **Function:**
 - Serializes 32-bit parallel data into 4-bit nibbles.
 - Outputs nibbles sequentially (LSB first).
 - Controls nibble sequencing and valid signaling.
 - Indicates busy status during serialization.
- **Input:**
 - `clk` - System clock
 - `rst_n` - Active-low reset
 - `data_in[31:0]` - Parallel data to be serialized
 - `data_valid` - Start serialization request
 - `cmd_busy` - Controller busy status
- **Output:**
 - `serial_out[3:0]` - Serialized output nibble
 - `serial_valid` - Output nibble valid
 - `serializer_busy` - Serializer busy indicator

`done_generator.sv`

- **Function:**
 - Detects completion of command execution.
 - Generates program-done pulse.
 - Differentiates success and error completion.
 - Controls pulse width based on error condition.
- **Input:**
 - `clk` - System clock
 - `rst_n` - Active-low reset
 - `cmd_start` - Command start indicator
 - `cmd_busy` - Command execution status
 - `cmd_error` - Error flag from controller
 - `cmd_error_type[1:0]` - Error classification
- **Output:**
 - `prog_done` - Program completion indicator

Testbench -

``timescale 1ns/1ps` - Simulation time unit and precision
`module testbench();` - Testbench top module
`reg clk;` - Clock

EC22B1004 - P Kaarthick Natesh

reg rst_n; - Active-low reset

reg [3:0] prog_nibble_in; - Serial 4-bit input

reg prog_nibble_in_valid; - input valid

wire [3:0] prog_nibble_out; - output nibble

wire prog_out_valid; - output valid

wire prog_done; - Program completion

wire [11:0] mem_addr; - Memory address

wire [31:0] mem_wdata; - Memory write data

wire [31:0] mem_rdata; - Memory read data

wire mem_wen; - Memory write enable

wire mem_cen; - Memory chip enable

cpu_top dut(...) - CPU DUT instantiation

memory mem_inst(...) - Memory model instantiation

always #50 clk = ~clk; - 100 ns clock generation

initial begin - Start stimulus

clk = 0; - Initialize clock

rst_n = 0; - Assert reset

repeat(4) @(negedge clk); - Hold reset

rst_n = 1; - Deassert reset

@(negedge clk); - Clock alignment

// Load 32'h12345678 to memory address 12'hF0 - CMD_WRITE

prog_nibble_in_valid = 1; - Start command

prog_nibble_in = 4'h0; - Address / opcode / data sequence

@(negedge clk); - Continue frame transmission

prog_nibble_in_valid = 0; - End command

repeat(2) @(negedge clk); - Wait

// Load 32'h87654321 to memory address 12'hF1 - CMD_WRITE

prog_nibble_in_valid = 1; - Start command

prog_nibble_in = 4'h1; - Address / opcode / data sequence

@(negedge clk); - Continue frame transmission

prog_nibble_in_valid = 0; - End command

repeat(2) @(negedge clk); - Wait

// Add mem(0xF2) = mem(0xF1) + mem(0xF0) - CMD_ADD

prog_nibble_in_valid = 1; - Start ADD command

prog_nibble_in = 4'h0; - Address / opcode sequence

repeat(8) @(negedge clk); - Dummy data padding

prog_nibble_in_valid = 0; - End command

repeat(2) @(negedge clk); - Wait

// Read mem(0xF2) - CMD_READ

prog_nibble_in_valid = 1; - Start READ command

prog_nibble_in = 4'h2; - Address / opcode sequence

repeat(8) @(negedge clk); - Dummy data padding

prog_nibble_in_valid = 0; - End command

```
repeat(2) @(negedge clk); - Wait
```

```
// Load 32'hFEDCBA98 to memory address 12'hF3 - CMD_WRITE
```

```
prog_nibble_in_valid = 1; - Start command
prog_nibble_in = 4'h3; - Address / opcode / data sequence
@(negedge clk); - Continue frame transmission
prog_nibble_in_valid = 0; - End command
repeat(2) @(negedge clk); - Wait
```

```
// Multiply {mem(0xF5),mem(0xF4)} = mem(0xF3) × mem(0xF2) - CMD_MUL
```

```
prog_nibble_in_valid = 1; - Start MUL command
prog_nibble_in = 4'h2; - Address / opcode sequence
repeat(8) @(negedge clk); - Dummy data padding
prog_nibble_in_valid = 0; - End command
repeat(2) @(negedge clk); - Wait
```

```
// Read mem(0xF4) - CMD_READ
```

```
prog_nibble_in_valid = 1; - Start READ command
prog_nibble_in = 4'h4; - Address / opcode sequence
repeat(8) @(negedge clk); - Dummy data padding
prog_nibble_in_valid = 0; - End command
repeat(2) @(negedge clk); - Wait
```

```
// Read mem(0xF5) - CMD_READ
```

```
prog_nibble_in_valid = 1; - Start READ command
prog_nibble_in = 4'h5; - Address / opcode sequence
repeat(8) @(negedge clk); - Dummy data padding
prog_nibble_in_valid = 0; - End command
repeat(18) @(negedge clk); - Allow serializer to finish
```

```
$stop; - Stop simulation
```

```
end - End stimulus
```

```
endmodule - End testbench
```

Running the testbench:

```
run -all
```

```
csh - Start C-shell
```


```
source /home/mentor/test.cshrc - Load Questa environment
```

```
vlog -64 +acc testbench.v memory.v serial_interface.v output_serializer.v
done_generator.v cpu_top.v cmd_controller.v - Compile design with full visibility
```


```
vsim -64 testbench -do "log -r /*" - Start simulation and log all signals
```

```
run -all - Run simulation
```

Schematic :

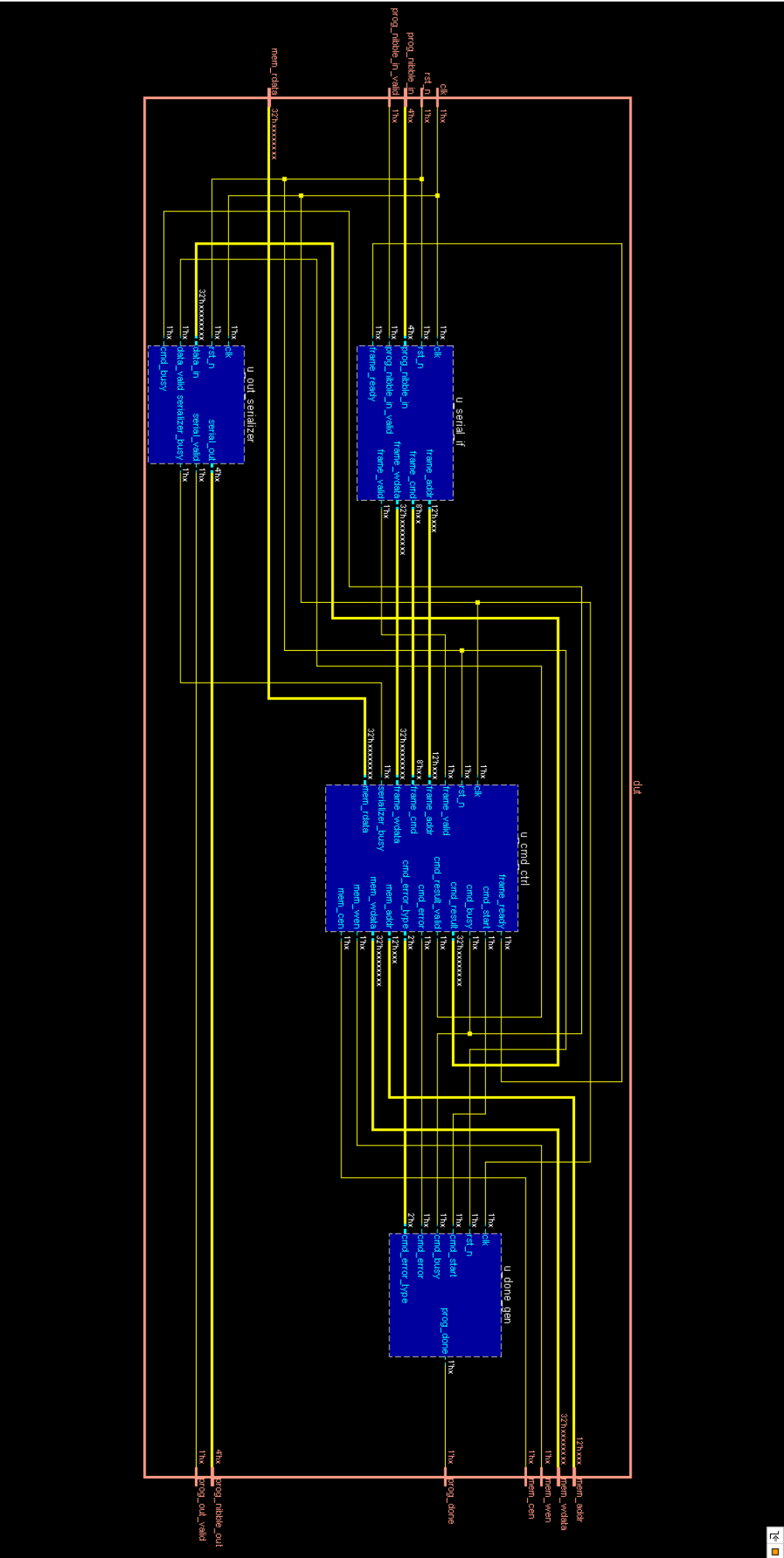


Output Waveforms:

 


1. Load 32'h12345678 to memory address 12'hF0 – CMD_WRITE

- 12'h0F0
- 8'h02
- 32'h12345678)

 

2. Load 32'h87654321 to memory address 12'hF1 - CMD_WRITE

- 12'h0F1
- 8'h02
- 32'h87654321

 


3. Add $\text{mem}(0x0F2) = \text{mem}(0x0F1) + \text{mem}(0x0F0) - \text{CMD_ADD}$

a. $12'h0F0$

b. $8'h10$

c. $32'hX$

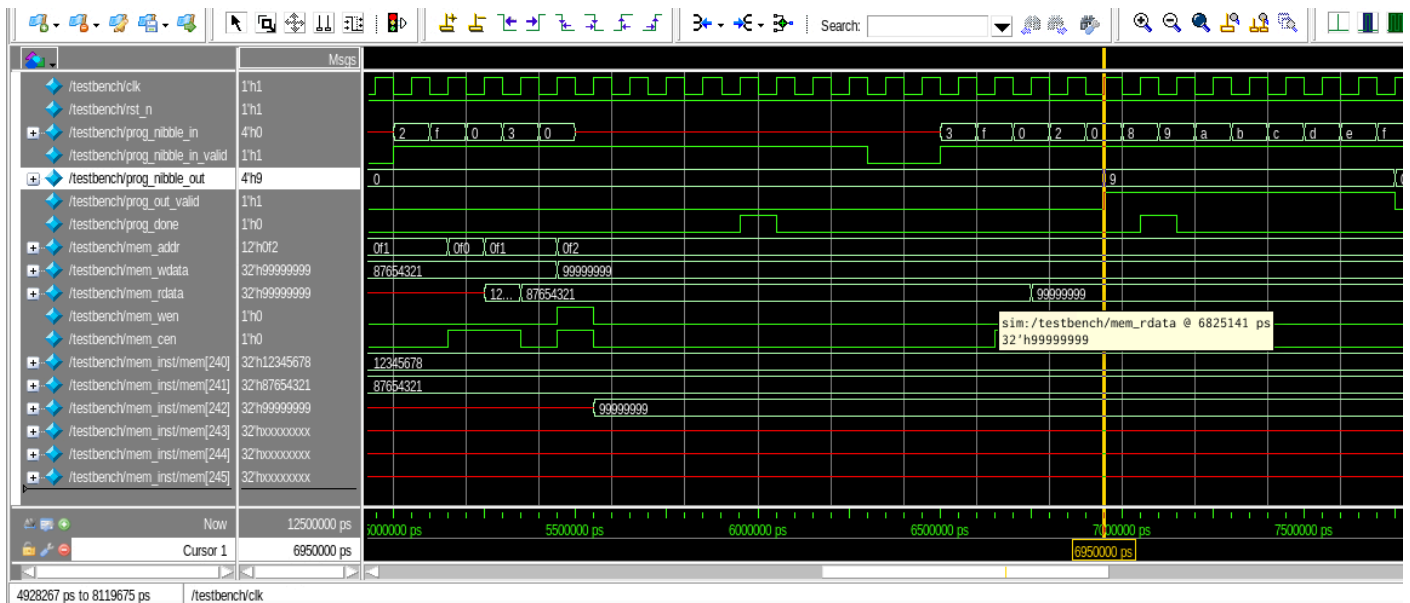i. $32'h12345678 + 32'h87654321 = 32'h99999999$




4. Read $\text{mem}(0xF2) - \text{CMD_READ}$

a. $12'h0F2$


b. $8'h03$

c. $32'hX$

 


5. Load 32'hfedcba98 to memory address 12'hF3 - CMD_WRITE

- 12'h0F3
- 8'h02
- 32'hfedcba98

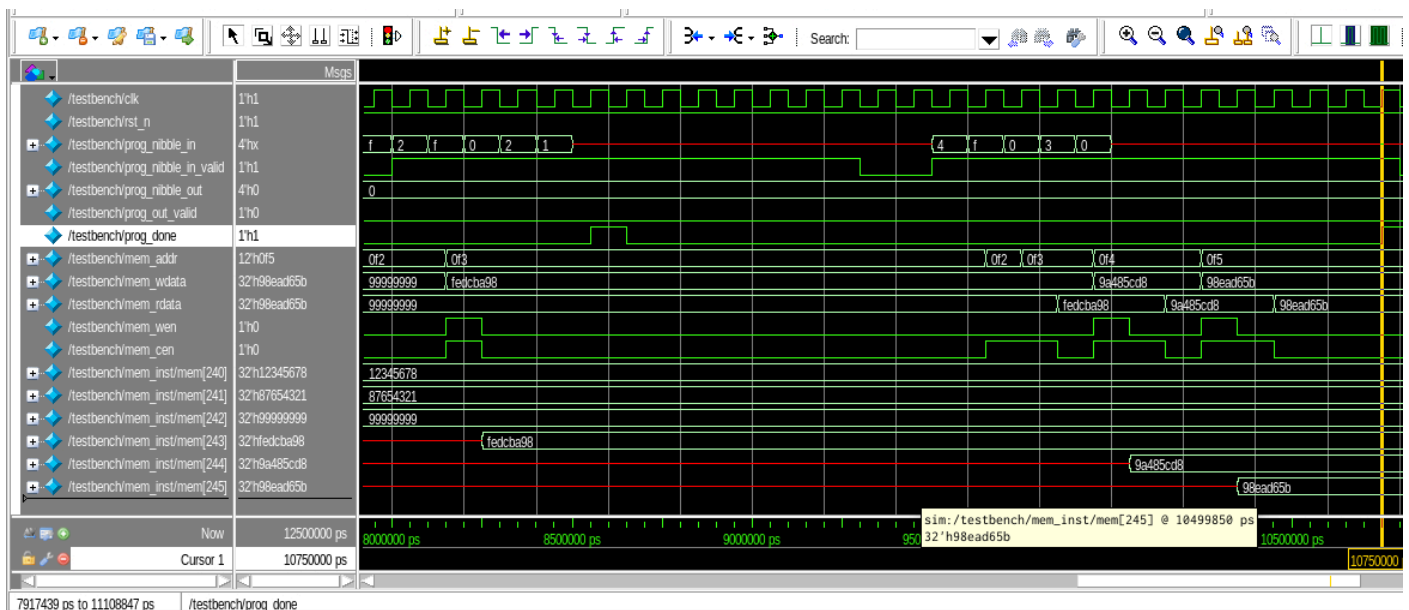

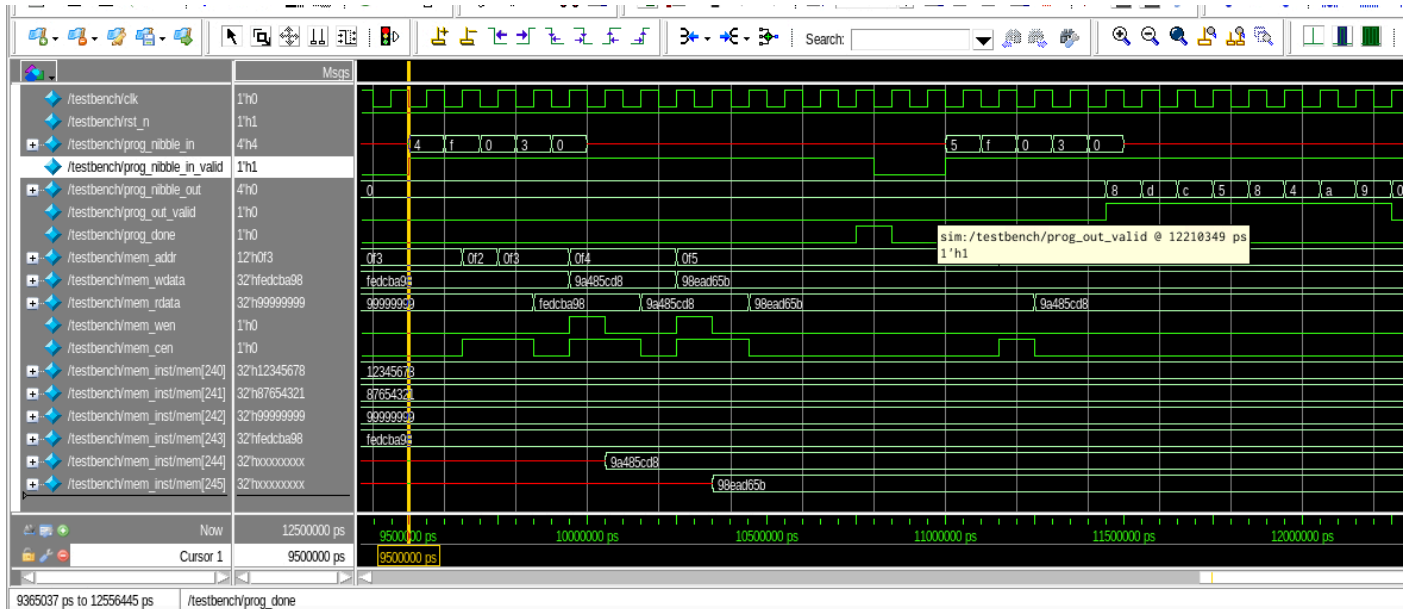
6. Multiply {mem(0xF5),mem(0xF4)} = mem(0x0F3) + mem(0x0F2) - CMD_MUL

- 12'h0F3
- 8'h12
- 32'hx
 - 32'h99999999 * 32'hfedcba98 = {32'h98ead65b, 32'h9a485cd8}
 - But from Calculator 32'h99999999 * 32'hfedcba98 = {32'h98ead65a, 32'h9a485cd8}



7. Read mem(0xF4) - CMD_READ

- 12'h0F4
- 8'h03
- 32'hX

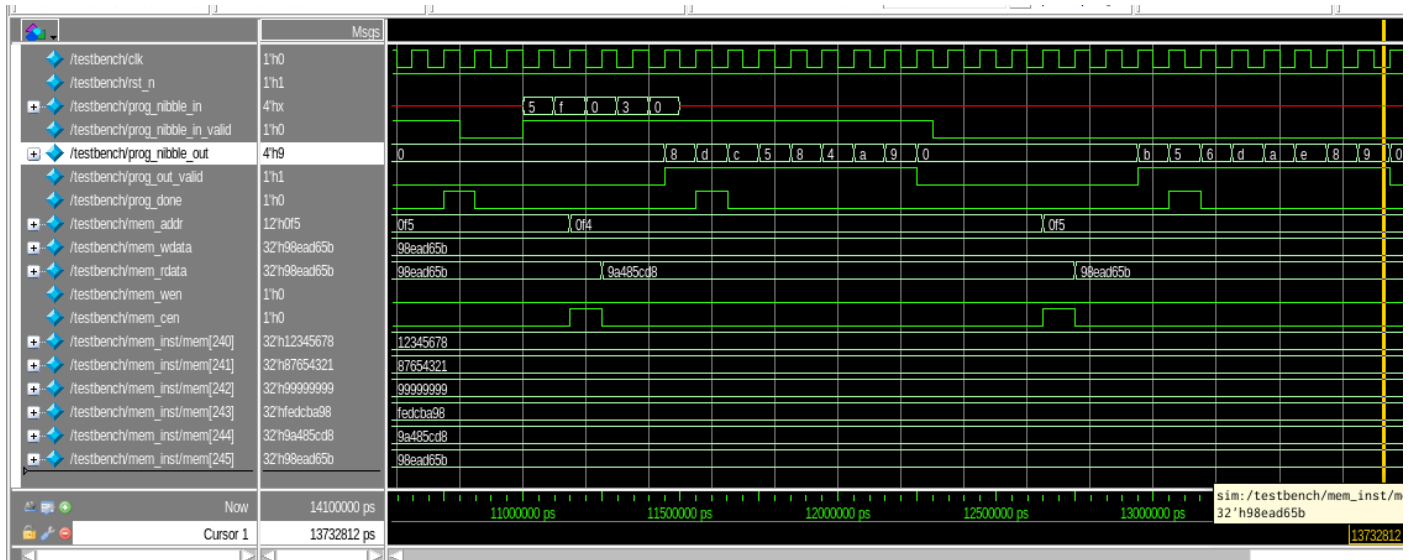

8. Read mem(0xF5) - CMD_READ

- 12'h0F2
- 8'h03
- 32'hX

Sources:

- questa_sim_ref.pdf
- questa_sim_gui.pdf
- A Verilog HDL Test Bench Primer - <https://people.ece.cornell.edu/land/courses/ece5760/Verilog/LatticeTestbenchPrimer.pdf>